

**Q.1 A Attempt the following**

**4 Marks**

- 1) Four adjacent minterm or maxterm makes one \_\_\_\_\_.
- 2) An n-bit register has a group of \_\_\_\_\_ flip flop.
- 3) Kmap is also known as \_\_\_\_\_.
- 4) Find the complement of :  $F = (A+B+C)(A'+B'+C)(AB'C')$

**Q.1 B Answer in brief (Any 1 out of 2)**


**2 Marks**

- 1) Simplify the Boolean expression :  $F = A+B'C(A+(B'(C)))$  with logic diagram
- 2) Define : Buffer Gate & Inverter Gate with truth table.

**Q.1 C Answer in detail (Any 1 out of 2)**

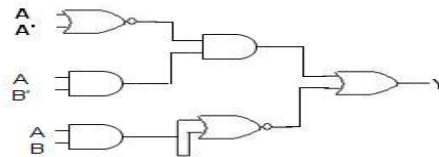**3 Marks**

What is the output Y for the logic circuit shown in the.1-→



- 2) Explain: DeMorgan's Law

**Q.1 D Write a note on (Any 1 out of 2)**

**5 Marks**

- 1) Simplify Boolean function using figure Kmap :  $F(x,y,z) = \Sigma (0,2,3,4,6)$
- 2) Explain: Universal Gates

**Q.2 A Attempt the following**

**4 Marks**

- 1) What is the new Improvement model for S-R flip flop?
- 2) VLSI = \_\_\_\_\_
- 3) Multiplexer is also known as \_\_\_\_\_
- 4) \_\_\_\_\_ is a basic element of sequential logic system.

**Q.2 B Answer in brief (Any 1 out of 2)**

**2 Marks**

- 1) Define: 2 to 4 line decoder
- 2) Define: 2 to 4 line Multiplexer

**Q.2 C Answer in detail (Any 1 out of 2)**

**3 Marks**

- 1) Short note on Register
- 2) Explain: Register with parallel Load with diagram

**Q.2 D Write a note on (Any 1 out of 2)**

**5 Marks**

- 1) Explain: Bi-Directional Shift Register
- 2) Explain: Ripple Counter

**Q.3 A Attempt the following**

**4 Marks**

- 1) Give meaning of m in formula  $n=m \cdot r$
- 2) The second name of the error detection code.
- 3) External interrupt come from \_\_\_\_\_ devices.
- 4) In the general register origination, the information from the output bus is received by

**Q.3 B Answer in brief (Any 1 out of 2)**

**2 Marks**

- 1) Perform multiplication  $1011 * 011 =$ \_\_\_\_\_.
- 2) What is parity bit ?

**Q.3 C Answer in detail (Any 1 out of 2)**

**3 Marks**

- 1) Find S,M,E in the given number :  $(-0.00010110)$
- 2) Perform multiplication  $110.110 * 10.10 =$ \_\_\_\_\_.

**Q.3 D Write a note on (Any 1 out of 2)**

**5 Marks**

- 1) Perform arithmetic operation  $(+42) + (-13)$  and  $(-42) - (-13)$  in binary using signed 2's

Complement representation for negative numbers.

2) Short note on : Floating-Point Representation

**Q.4 A Attempt the following**

**4 Marks**

- 1) In the general register organization, the information from the output bus is received by\_\_\_\_\_.
- 2) \_\_\_\_\_ performs the required micro operation in CPU.
- 3) \_\_\_\_\_ register capable to perform an addition and store result into itself.
- 4) \_\_\_\_\_ interrupts initiated by an illegal or errorneous use of an instruction.

**Q.4 B Answer in brief (Any 1 out of 2)**

**2 Marks**

- 1) Give Reverse Polish Notation of:  $A+B*[C*D+E*(F+G)]$
- 2) Define: Working of ALU with diagram.

**Q.4 C Answer in detail (Any 1 out of 2)**

**3 Marks**

- 1) Explain: Accumulator Organization
- 2) Explain: Types of Interrupts

**Q.4 D Write a note on (Any 1 out of 2)**

**5 Marks**

- 1) Explain: General Register Organization
- 2) Write a sequence of microoperations for PUSH and POP in a 64-word stack.

**Q.5 A Attempt the following**

**4 Marks**

- 1) \_\_\_\_\_ register holds the number of words to be transferred and decremented by one.
- 2) Each peripheral device has associated with their \_\_\_\_\_ to communicate with I/O buses.
- 3) True or False: CPU has limited data transfer speed between main memory & secondary memory.
- 4) A special kind of processor designed to facilitate I/O instruction is called \_\_\_\_\_.

**Q.5 B Answer in brief (Any 1 out of 2)**

**2 Marks**

- 1) How many methods of transfer take place in DMA?
- 2) Mention the application of DMA.

**Q.5 C Answer in detail (Any 1 out of 2)**

**3 Marks**

- 1) Explain different modes of transfer between CPU & I/O Devices.
- 2) Draw the block diagram of memory buses & explain how they communicate with peripheral & CPU.

**Q.5 D Write a note on (Any 1 out of 2)**

**5 Marks**

- 1) Explain: IOP
- 2) Explain: DMA Controller